



A Small, Cheap and Easy to Build Solar Energy System


**Author: Nguyễn Thanh Duy
Tân
Amateur**

General Informations of this project

The solar energy system project has 3 main points, described as the diagram



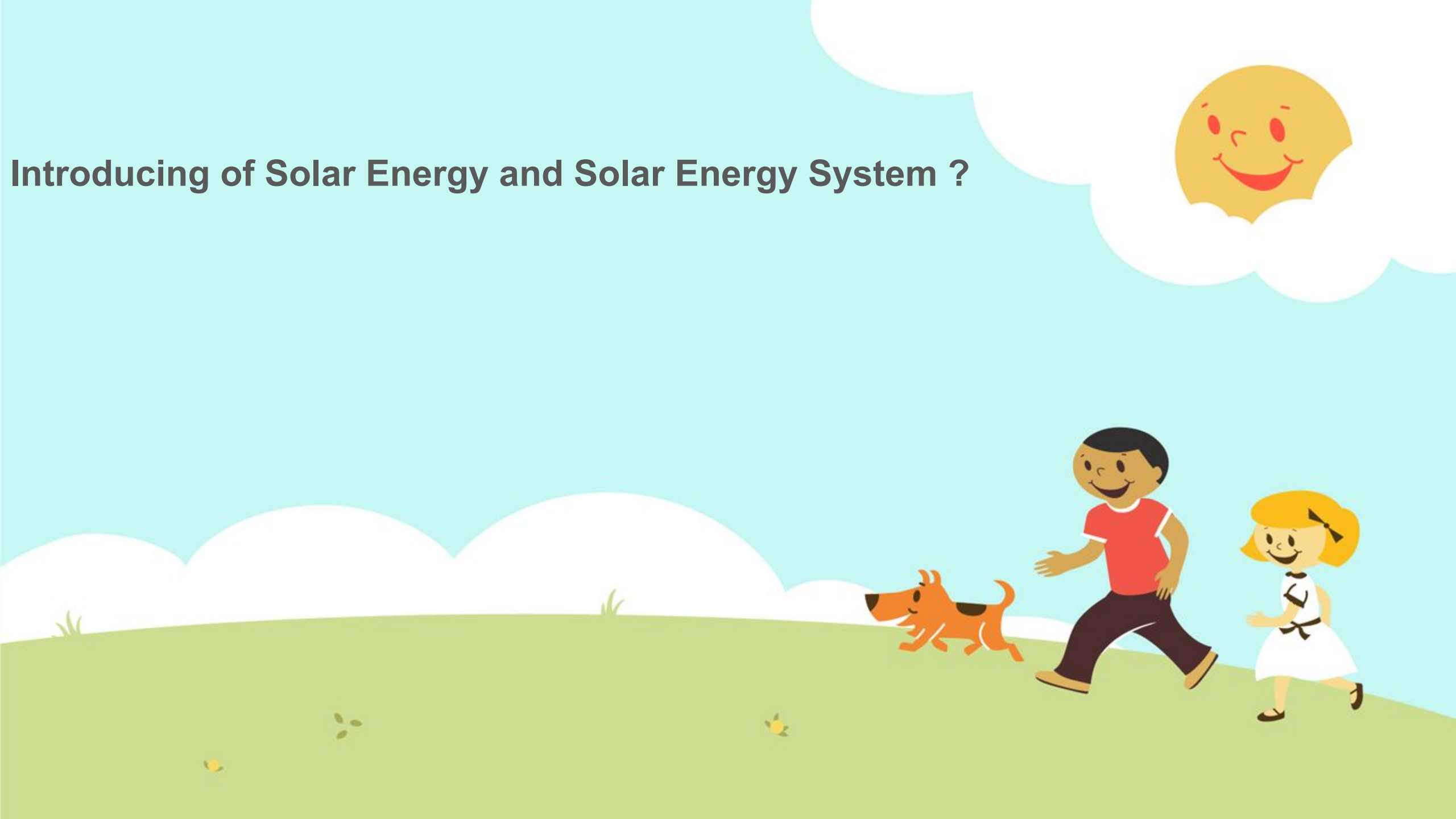
Introducing of Solar Energy and Solar Energy System ?



Which functions provided by this solar energy system ?

- Providing energy for charging battery packs
- Using batteries charged for powering low-energy consuming devices like LED bulbs, Fans, charging mobiles/tablet, small speakers, or things else use low-voltage from 5-12V
- Allowing monitor and control process of charging battery packs from solar panels via Android App and Web Server or Bluetooth Communication
- Allowing on/off devices linked to system by relays
- Allowing expand storage capacity by adding more battery packs later

System's General Operation Diagram

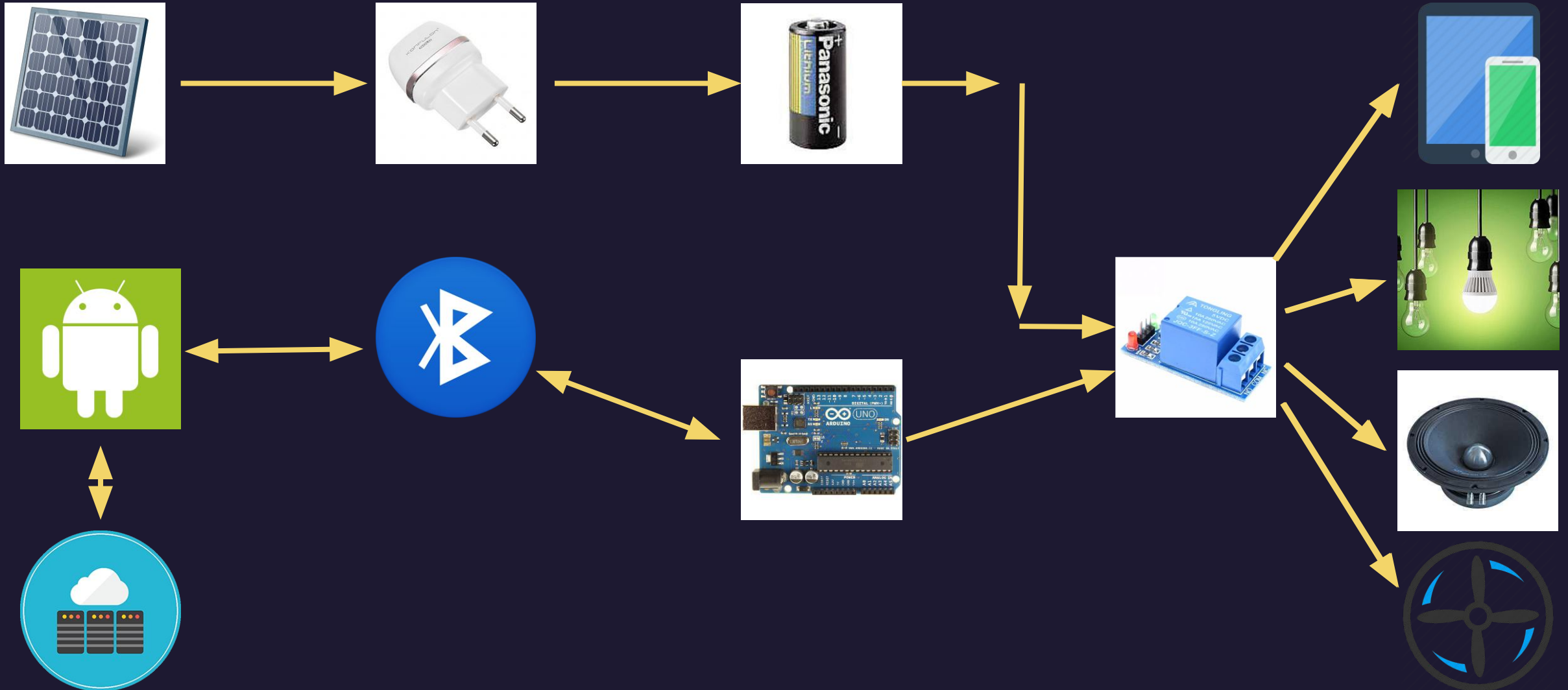

Needed parts for building this project are

NAME	PRICE	NUMBER	NOTES
Small, cheap 0.35W - 5.5V -65mA Solar Panels	~1\$ per one	4	
18650 Batteries 1100mAh	~1.5\$ per one	2	just 2 for using in this demo
Bluetooth Module HC06	~5\$ per one	1	
Uno Arduino Board	~9\$ per one	1	Any Arduino Board else is available for this project
Some Relays	~0.4\$ per one	4	just 4 for using in this demo
Charger Board/Module allows charge 18650 batteries	~0.8\$ per one	1	just 1 for using in this demo
Some 3W-4V LEDs	~0.8\$ per one	2	just 2 for using in this demo
12V – Speaker Module	~4\$ per one	1	


Count:	~30-35\$ (included wires, buzzer, solder materials,etc
--------	--

Choosing Solar Panels

This is solar panels used for this demo



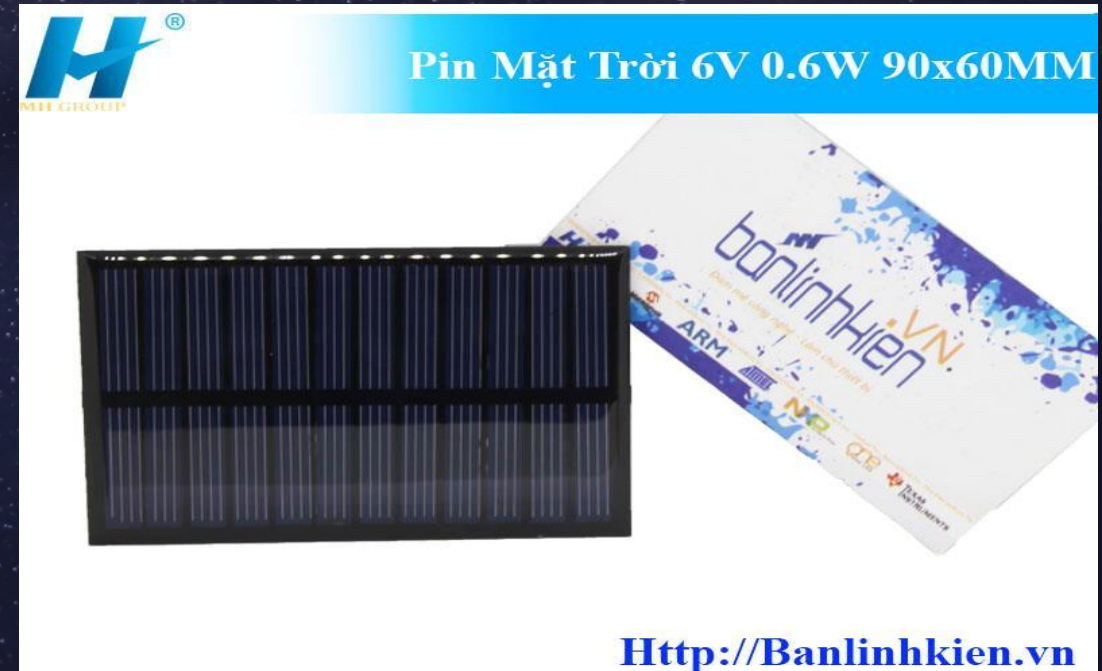Another one provides higher capacity but still be cheap and small solar panel (0.6W – 6V – 100mA. The price per one is ~1.7\$



Connecting Solar Panels Together

2 Basic Ways of Connecting

The way uses combined both

In Series



Output: 11V – 65mA

Output: 5.5V – 130mA

Output: 11V – 130mA

Better Output: 12V – 200mA if 6V Panels Used

In Parallel



Choosing Battery

The battery cell used in this demo are Panasonic 18650 batteries which have capacity ~1100mAh/one




About reading and understand details printed on battery:

- Example: 1100mAh 2A 3.7V


- + Available Capacity: 1100mAh means this battery can provide constantly a current at 1100mA/1.1A for an hour, this depends on how much current of device connecting to battery uses. So if we have an device need 550mA to operate, this battery can last for 2 hrs


- + Max Current Available: 2A is the max current battery can provide in a short time

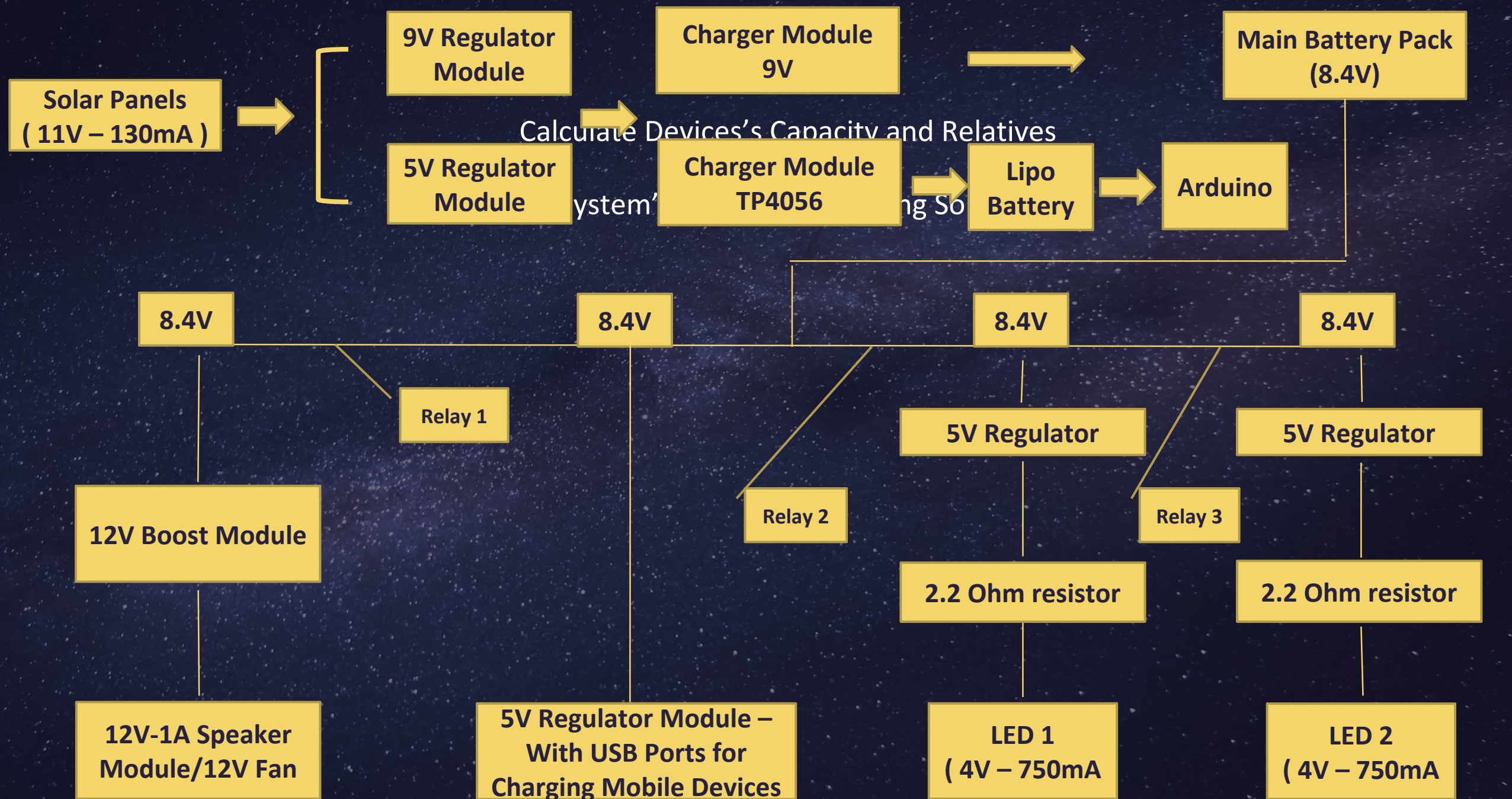
- + Voltage: 3.7V is the stable voltage of battery when it works and 4.2V is the voltage when it fully charged




Wiring Components to Arduino

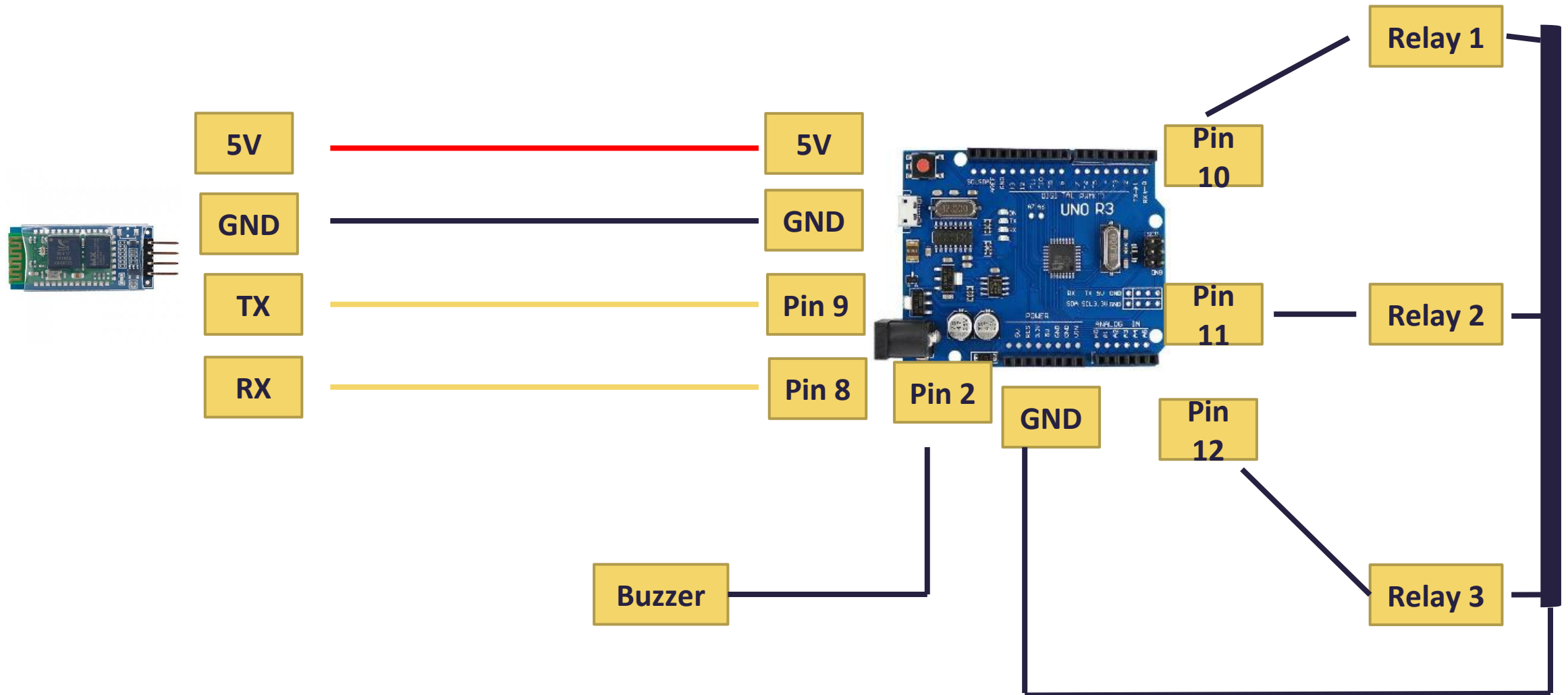

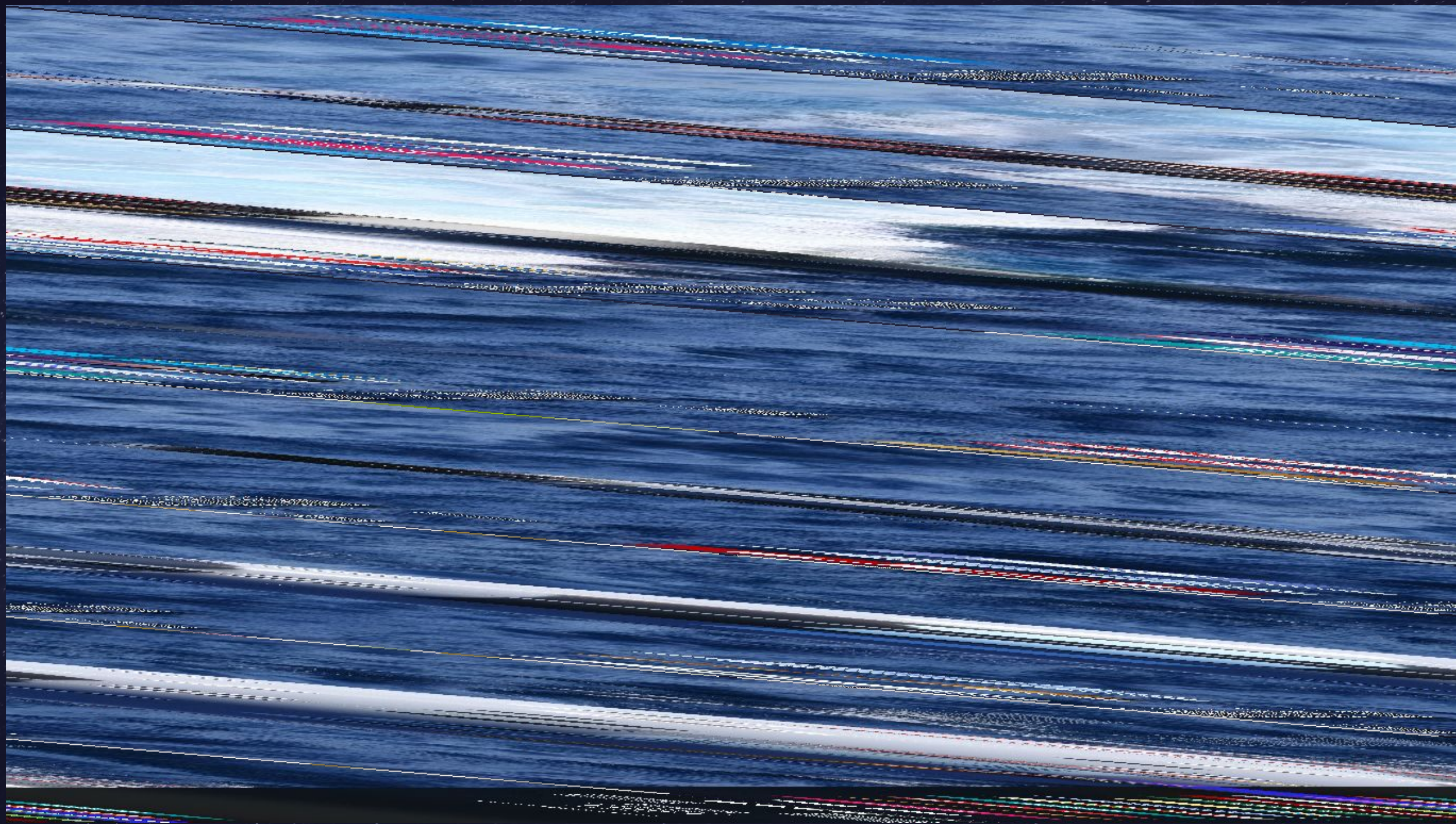

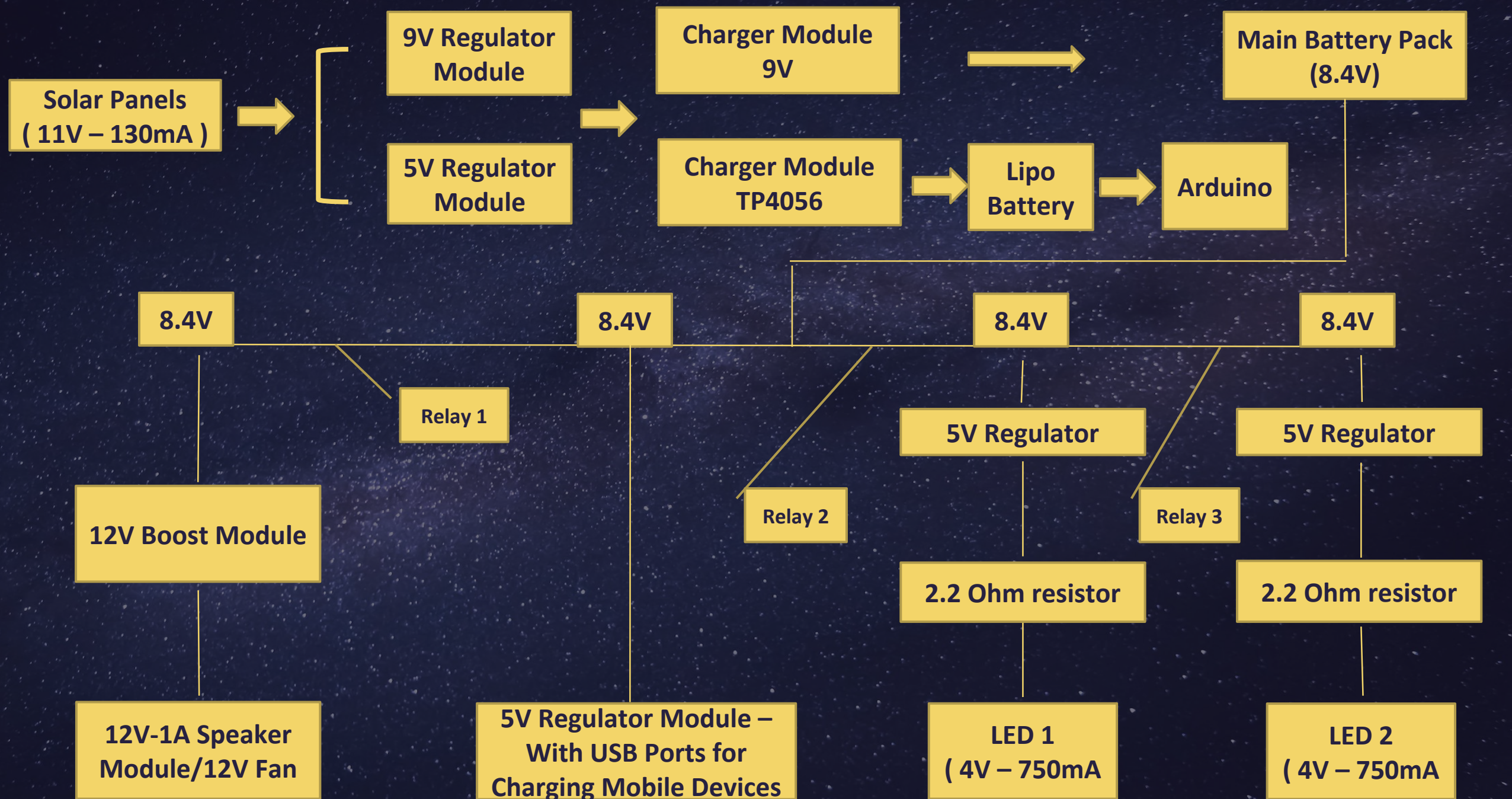

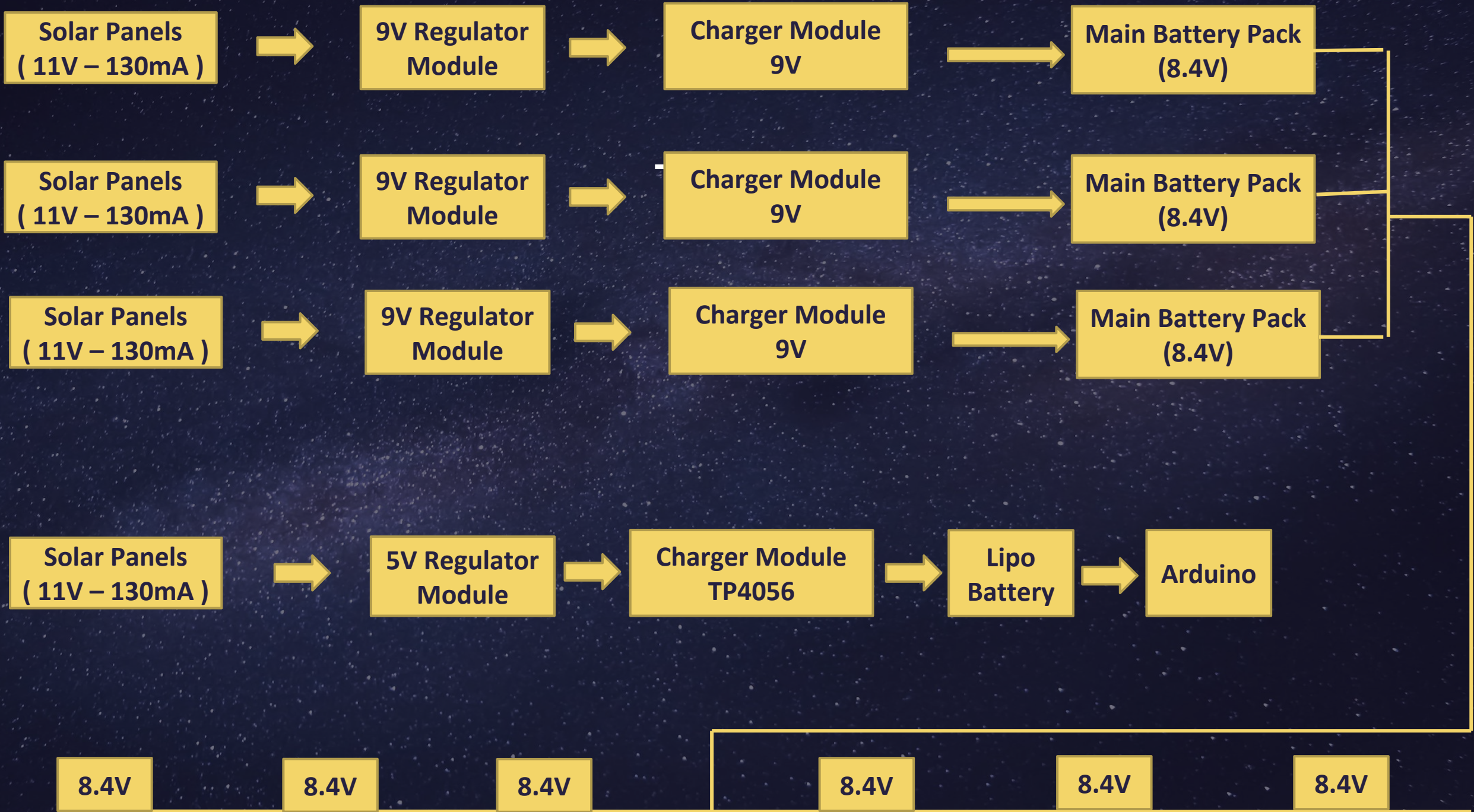

thanks for listening

Email: cozmo178212@gmail.com

FB: Nguyễn Thanh Duy Tân